

Transient Issues:

1. We know how to derive the coupled wave equations for V and I. For the lossless case we have:

$$\frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t} \text{ and } \frac{\partial I}{\partial z} = -C \frac{\partial V}{\partial t}$$

Please note that $V = V(z,t)$ and $I = I(z,t)$

2. We can decouple these and get the wave equation

$$\frac{\partial^2}{\partial z^2} \begin{Bmatrix} V \\ I \end{Bmatrix} = LC \frac{\partial^2}{\partial t^2} \begin{Bmatrix} V \\ I \end{Bmatrix}$$

3. We assume:

$$\begin{aligned} V(z,t) &= V^+(z,t) + V^-(z,t) \\ I(z,t) &= I^+(z,t) + I^-(z,t) \end{aligned}$$

Which means:

- a) Each V and I at any point on the line at any time is generally a linear combination superposition of the positive and negative traveling waves.
- b) A positive traveling wave means that the wave is going in the +z direction. V^+ means that voltage is going to +z and it can be negative or positive in magnitude.
- c) Always be careful about I. Generally speaking I^+ is a current going to the +z direction and I^- is a current going to the -z direction.
- d) While I is a scalar, it has a kind of direction associated with it.

If 2A goes to +z and 2A goes to -z at (z_1, t_1) , we know that the net current at (z_1, t_1) is 0. So while I is a scalar, the direction +z vs. -z needs to be considered.

- 4.

$$\left. \begin{aligned} V(z,t) &= V^+\left(t - \frac{z}{u}\right) + V^-\left(t + \frac{z}{u}\right) \\ I(z,t) &= I^+\left(t - \frac{z}{u}\right) + I^-\left(t + \frac{z}{u}\right) \end{aligned} \right\} \text{ These are the general definitions assuming no functional form.}$$

$$\frac{\partial V}{\partial z} = -\frac{1}{u} V^+\left(t - \frac{z}{u}\right)' + \frac{1}{u} V^-\left(t + \frac{z}{u}\right)'$$

$$\frac{\partial V}{\partial t} = V^+\left(t - \frac{z}{u}\right)' + V^-\left(t + \frac{z}{u}\right)'$$

$u = \text{phase speed} \rightarrow \text{speed for constant phase}$

$$\frac{\partial}{\partial t}(t - \frac{z}{u}) = 0 \rightarrow \frac{+1}{u} \frac{\partial z}{\partial t} = 1 \rightarrow \frac{\partial z}{\partial t} = u \rightarrow + \text{traveling}$$

$$\frac{\partial}{\partial t}(t + \frac{z}{u}) = 0 \rightarrow \frac{\partial z}{\partial t} = -u \rightarrow - \text{traveling}$$

$$\frac{\partial I}{\partial z} = -\frac{1}{u} I^{+'}(t - \frac{z}{u}) + \frac{1}{u} I^{-'}(t + \frac{z}{u})$$

$$\frac{\partial I}{\partial t} = I^{+}(t - \frac{z}{u}) + I^{-'}(t + \frac{z}{u})$$

Note 1:

$$\frac{\partial V^{+}(t - \frac{z}{u})}{\partial z} = \frac{\partial V^{+}(t - \frac{z}{u})}{\partial(t - \frac{z}{u})} \frac{\partial(t - \frac{z}{u})}{\partial z} = -\frac{1}{u} V^{+'}(t - \frac{z}{u})$$

$$\frac{\partial V^{-}(t + \frac{z}{u})}{\partial z} = \frac{\partial V^{-}(t + \frac{z}{u})}{\partial(t + \frac{z}{u})} \frac{\partial(t + \frac{z}{u})}{\partial z} = \frac{1}{u} V^{-'}(t + \frac{z}{u})$$

This note defines $V^{+'}$, $V^{-'}$, $I^{+'}$, and $I^{-'}$

$$5. \frac{\partial V}{\partial z} = -L \frac{\partial I}{\partial t} \rightarrow \frac{-1}{u} V^{+'} + \frac{1}{u} V^{-'} = -L(I^{+'} + I^{-'}) \rightarrow \boxed{I^{+} + I^{-} = \frac{V^{+'}}{uL} - \frac{V^{-'}}{uL}}$$

Note: The equation written above is important!

a) The + traveling items $I^{+'} = \frac{V^{+'}}{uL}$ should match

b) The – traveling items $I^{-'} = -\frac{V^{-'}}{uL}$ should match

By integration one can see (note: at $t = 0$, I and V don't exist), it is the same relation as $I^{+} = \frac{V^{+}}{uL}$ and $I^{-} = -\frac{V^{-}}{uL}$.

6.

$$\frac{\partial I}{\partial z} = -C \frac{\partial V}{\partial t}$$

$$-\frac{1}{u} I^{+'} + \frac{1}{u} I^{-'} = -C(V^{+'} + V^{-'})$$

$$\rightarrow I^{+'} + I^{-'} = uCV^{+'} - uCV^{-'}$$

Again, we can see that: $I^{+} = uCV^{+}$ and $I^{-} = -uCV^{-}$.

$$7. \text{ So a) } uC = \frac{1}{uL} \rightarrow u^2 = \frac{1}{LC} \rightarrow u = \frac{1}{\sqrt{LC}}$$

$$\text{b) } uC = \sqrt{\frac{C}{L}} \text{ and } uL = \sqrt{\frac{L}{C}}$$

$$\therefore I^{+} = \frac{V^{+}}{\sqrt{\frac{L}{C}}} \text{ and } I^{-} = -\frac{V^{-}}{\sqrt{\frac{L}{C}}} \rightarrow \sqrt{\frac{L}{C}} = R_o \text{ (Characteristic Impedance)}$$

$$\Rightarrow I^{+} = \frac{V^{+}}{R_o} \text{ and } I^{-} = -\frac{V^{-}}{R_o}$$

8. Two important items:

$$\text{a) } R_o = \sqrt{\frac{L}{C}} \text{ comes out of the equation and is characteristic impedance}$$

** R_o is a special ratio of L and C and relates V to I on positive and negative traveling waves**

$$\text{b) } I^{-} = -\frac{V^{-}}{R_o}$$

This – comes out of the formulation and makes physical sense.


If I^{+} is going +z, it will be > 0 . The same going to –z will be < 0 .

As you can see, while current is a scalar, there's a direction (direction of moving charges) associated with it.

Note: By unit analysis, $R_o = \sqrt{\frac{L}{C}} \Rightarrow \text{ohms}$; this is like a load. Even in a lossless line, the way we balance energy between series inductance and shunt capacitance acts like a loading factor R_o which is called characteristic impedance.

9. Reflection Coefficients:

a) At the load:

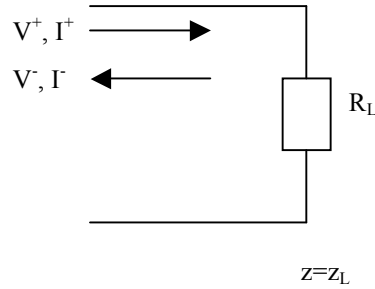

At $z=z_L$ and $t = \tau$,

$$\frac{V_{Total}}{I_{Total}} = R_L = \frac{V^+(z_L, \tau) + V^-(z_L, \tau)}{I^+(z_L, \tau) + I^-(z_L, \tau)} \rightarrow \frac{V^+(z_L, \tau)}{I^+(z_L, \tau)} \frac{1 + \frac{V^-(z_L, \tau)}{V^+(z_L, \tau)}}{1 + \frac{I^-(z_L, \tau)}{I^+(z_L, \tau)}}$$



$\uparrow R_0$

$$\text{Reflection Coefficient} = \Gamma = \frac{\text{Reflected}}{\text{Transmitted}} = \frac{V^-}{V^+}$$

$$\Gamma_L = \Gamma_{at\ load} = \frac{V_L^-}{V_L^+} \text{ and } \frac{I_L^-}{I_L^+} = \frac{-\frac{V_L^-}{R_0}}{\frac{V_L^+}{R_0}} = -\Gamma_L$$

$$R_L = R_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} \rightarrow \boxed{\Gamma_L = \frac{R_L - R_0}{R_L + R_0}} = \frac{V^-}{V^+} \text{ at } z=z_L$$

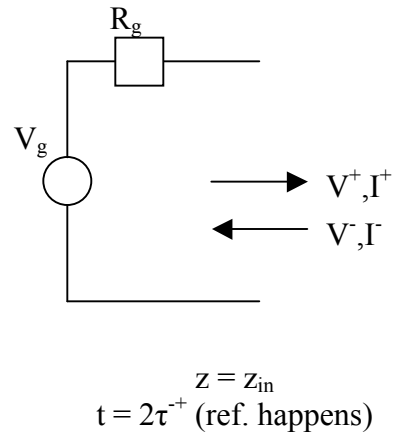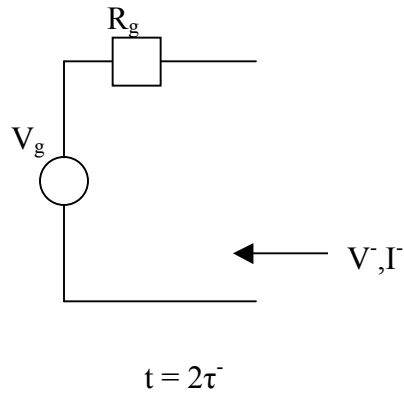What about $t = 2\tau$, when the wave reaches the load and bounces back to get back to the $z=z_{in}$ position?




$$\Gamma_g = \frac{V^+(z = z_{in})}{V^-(z = z_{in})} \text{ for transient the inc. is } V^- \text{ and reflected is } V^+$$

Note: If $V_g \rightarrow 0$ at $t = 2\tau \Rightarrow$ the source was a pulse

$$\text{Then, at } z = z_{il} + \frac{V(z_{in}, 2\tau^+)}{I(z_{in}, 2\tau^+)} = R_g$$

$$+ \frac{\frac{V^+}{R_o} + \frac{V^-}{R_o}}{\frac{V^+}{R_o} - \frac{V^-}{R_o}} = R_g$$

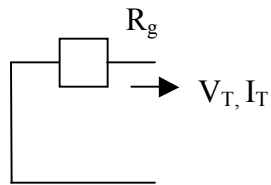
$$+ \frac{\frac{V(\Gamma_g + 1)}{R_o}}{\frac{V}{R_o}(\Gamma_g - 1)} = R_g$$



at $z = z_{in}$

$$R_o \left(\frac{\Gamma_g + 1}{\Gamma_g - 1} \right) = R_g \Rightarrow \Gamma_g = \frac{R_g - R_o}{R_g + R_o} = \frac{V^+}{V^-}$$

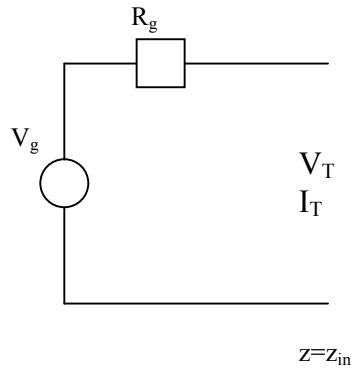The difficulty of the conceptual picture arises when we need to include V_g .



$$Z=Z_{in}$$

$$t = 2\tau^+$$

$$V_g - V_T = I_T R_g$$

$$V_g - (V^+ + V^-) = (I^+ + I^-) R_g$$

$$V_g - V^+ \left(1 + \frac{1}{\Gamma_g}\right) = \frac{V^-}{R_o} \left(1 - \frac{1}{\Gamma_g}\right) R_g$$

$$V^+ \left[\frac{R_g}{R_o} - \frac{R_g}{R_o \Gamma_g} + 1 + \frac{1}{\Gamma_o} \right] = V_g$$

$$V^+ \left[\frac{R_g}{R_o} + 1 - \frac{1}{\Gamma_o} \left(\frac{R_g}{R_o} - 1 \right) \right] = V_g$$

$$V^+ \left[1 - \frac{1}{\Gamma_o} \frac{\frac{R_g}{R_o} - 1}{\frac{R_g}{R_o} + 1} \right] = \frac{V_g}{\frac{R_g}{R_o} + 1}$$

$$V^+ - V^+ \frac{V^-}{V^+} \frac{R_g - R_o}{R_g + R_o}$$

At $t = 2\tau^+$, $Z=Z_{in}$

$$V^+ = V_g \frac{R_o}{R_o + R_g} + \frac{R_g - R_o}{R_g + R_o} V^-$$

Total + traveling voltage at $t = 2\tau^+$. This is going towards the load.

This is the contribution to V^+ due to V_g (which is on at $t = 2\tau^+$). V_{1a}^+ is at $t = 0^+$

This is the contribution due to V^- (coming toward) the generator.

Let us focus on:


$$\frac{R_g - R_o}{R_g + R_o} V^-$$

But we know, $\Gamma_g = \frac{V^+}{V^-} \rightarrow V_{\text{due to reflection}}^+ = \Gamma_g V^-$

$$\rightarrow \boxed{\Gamma_g = \frac{R_g - R_o}{R_g + R_o}} = \frac{V^+}{V^-} \bigg|_{z=z_{in}} \quad \text{This is a transient phenomenon!}$$

Transient Thinking and Concepts Continued...

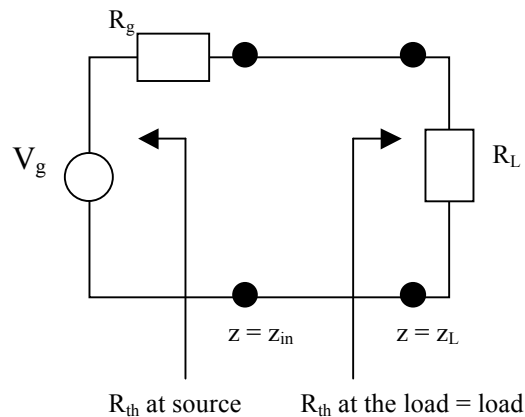Note: Reflection coefficient at the load = $\Gamma_L = \frac{R_L - R_o}{R_L + R_o} = \frac{V^-}{V^+}$



$$\Gamma_g = \text{reflection coefficient at the generator} = \frac{V_{z=z_{in}}^+}{V_{z=z_{in}}^-} = \frac{R_g - R_o}{R_g + R_o}$$

R_L = is the effective load at $z = z_L$ looking toward the load (to z^+)

R_g = is the Thevenin Equivalent R_{th} of the generator. This means at $z = z_{in}$ to find R_g , one needs to look into the source (generator) at the input (to z^-).

Power Discussion:

At any point in time and space (z_1, t_1) , we can calculate power as:

$$\begin{aligned}
 P(z_1, t_1) &= V_{Total}(z_1, t_1) I_{Total}(z_1, t_1) \\
 &= [V^+(z_1, t_1) + V^-(z_1, t_1)][I^+(z_1, t_1) + I^-(z_1, t_1)] \\
 &= \underbrace{V^+(z_1, t_1)I^+(z_1, t_1)}_1 + \underbrace{V^-(z_1, t_1)I^-(z_1, t_1)}_2 + \underbrace{V^+(z_1, t_1)I^-(z_1, t_1)}_3 + \underbrace{V^-(z_1, t_1)I^+(z_1, t_1)}_4
 \end{aligned}$$

1) This is + traveling power = $V^+ I^+ = \frac{V^+ V^+}{R_o} = \frac{V^{+2}}{R_o} = R_o I^{+2}$ always positive

2) This is – traveling power = $V^- I^- = V^- \left(-\frac{V^-}{R_o} \right) = -\frac{V^{-2}}{R_o} = -R_o I^{-2}$ always negative

3) & 4) are mixed terms:

$$V^+ I^- + V^- I^+ = V^+ \left(-\frac{V^-}{R_o} \right) + V^- \left(\frac{V^+}{R_o} \right) = 0 \quad \text{The cross terms add to 0!}$$

$$\Rightarrow P_{Total} = P^+ + P^- \text{ at all } (z, t)$$

$$P^+ = \frac{V^{+2}}{R_o}$$

$$P^- = -\frac{V^{-2}}{R_o}$$

As you can see,
 $P^+ > 0$ and $P^- < 0$
which means
power also has
direction.