

Game 4/22/20 T-line voltage and current


**For this problem, you need to show your work in detail. Have clear presentation**

For the following T-line system you know  $Z_L=150$  ohms  $Z_0=50$  ohms and the length of the line is

$\frac{13\lambda}{2}$  this means that  $x_{in} = -\frac{13\lambda}{2}$  since the load is at  $x=0$ .

If you know that  $V^+(x=0) = 5$  volts

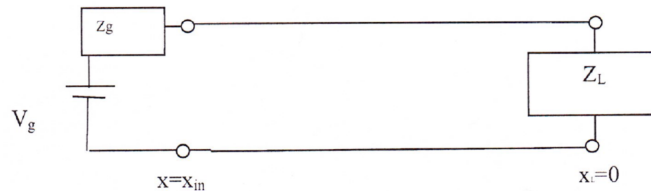- Find  $V^-$
- Find  $I$  at  $x=0$
- Find  $Z_{in}$  which is the impedance at  $x = x_{in}$
- Find  $V^-$  at  $x = x_{in}$
- Find  $I^-$  at  $x = x_{in}$



a) Reflection coefficient  $\Gamma(0) = \frac{150-50}{150+50} = \frac{1}{2} \rightarrow \frac{V^-(0)}{V^+(0)} = \Gamma(0) \rightarrow \frac{V^-(0)}{5} = \frac{1}{2}$  so.  $V^-(0) = 2.5$  V

b) We have two ways to do this let us try both

a. Knowing  $V^+(0) = 5 \rightarrow \frac{V^+(0)}{z_0} = I^+(0) = \frac{1}{10}$  A.  $I^-(0) = -\Gamma(0)I^+(0) = -\frac{1}{20}$

Knowing  $I^+(0)$  we can find  $I(0) = I^+(0) + I^-(0) = I^+(0) - \Gamma(0)I^+(0) = \frac{1}{10} - \frac{1}{20} = \frac{1}{20} = I(0)$

Check answer, verify consistency.  $V(0) = V^+(0) + V^-(0) = 7.5 \rightarrow I(0) = \frac{V(0)}{Z_L} = \frac{7.5}{150} \rightarrow I(0) = \frac{1}{20}$  Checked

c)  $Z_{in} = Z(x_{in}) = z_0 \frac{1+\Gamma(0)e^{j2\beta x_{in}}}{1-\Gamma(0)e^{-j2\beta x_{in}}} = 50 \frac{1+\frac{1}{2}e^{j2\frac{2\pi}{\lambda}(-\frac{13\lambda}{2})}}{1-\frac{1}{2}e^{-j2\frac{2\pi}{\lambda}(-\frac{13\lambda}{2})}} = 150 \text{ Ohms} = Z_{in}$

as we know every half wavelength it repeats

d)  $V^-(x_{in}) = V^-\left(-\frac{13\lambda}{2}\right) = V^-(0)e^{-j\frac{2\pi}{\lambda}(-\frac{13\lambda}{2})} = -2.5 \text{ V} = V^-(x_{in})$

e) Technically at any point  $I^-(x_{in}) = -\frac{V^-(x_{in})}{z_0} = -\frac{-2.5}{50} = \frac{1}{20} \text{ A} = I^-(x_{in})$

Another way  $I^-(x_{in}) = I^-\left(-\frac{13\lambda}{2}\right) = I^-(0)e^{-j\frac{2\pi}{\lambda}(-\frac{13\lambda}{2})} = -\frac{1}{20} \text{ A} = I^-(x_{in})$

EE311  
Spring 2020

Name \_\_\_\_\_  
Code \_\_\_\_\_

Game 4/22/20 T-line voltage and current