

Game 4/27/20 T-line voltage and current


To GET FULL CREDIT FOR THIS PROBLEM, YOU NEED TO GET HAVE YOUR RESULTS (without exponentials

such as  $e^{j\frac{5\pi}{2}}$  or  $e^{j\frac{18\pi}{4}}$  etc.

For the following T-line system, you know  $Z_L=100$  ohms  $Z_0=50$  ohms  $Z_g=150$  ohms and the length of the line is  $\frac{755\lambda}{4}$

If you know that  $V^-(x_{in} = -\frac{755\lambda}{4})$  is 20 volts

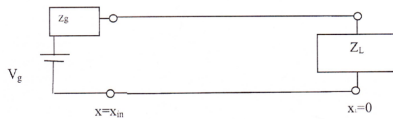- Find  $V^+$  and total  $I$  at the input of the line ( $x_{in} = -\frac{755\lambda}{4}$ )
- Find  $I^-$  at the load positions ( $x=0$ )
- Find the average power at the input of the line ( $x_{in} = -\frac{755\lambda}{4}$ )
- Can you find  $V_g$ ? Explain and show if you can or cannot and find it if you think you can



- To do this the easiest way is to find  $Z_{in}$

- $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3}$
- $Z_{in} = Z(x_{in} = -\frac{755\lambda}{4}) = Z_0 \frac{1 + \Gamma_L e^{j\frac{4\pi}{\lambda}(-\frac{755\lambda}{4})}}{1 - \Gamma_L e^{j\frac{4\pi}{\lambda}(-\frac{755\lambda}{4})}} = Z_0 \frac{1 - j\Gamma_L}{1 + j\Gamma_L} = Z_0 \frac{1 - j\frac{1}{3}}{1 + j\frac{1}{3}} = \frac{Z_0^2}{Z_L} = \frac{50^2}{100} = 25\Omega = Z_{in}$
- $\Gamma(x_{in} = -\frac{755\lambda}{4}) = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3} = \Gamma_{in}$
- $\Gamma_{in} = \frac{V_{in}^-}{V_{in}^+}$  so  $V_{in}^+ = 20(\frac{1}{-1/3}) = -60V$
- $I_{in} = \frac{V_{in}^-}{Z_0} = \frac{-40}{25} = -1.6A = I_{in}^-$   $I_{in}^+ = -\frac{V_{in}^-}{Z_0} = -\frac{20}{50} = -0.4A$
- $I_L^- = I_{in}^- e^{j\beta(\frac{755\lambda}{4})} = I_{in}^- e^{j\frac{2\pi}{\lambda}(\frac{755\lambda}{4})} = I_{in}^- e^{j\pi(\frac{755}{2})} = -0.4e^{j(\frac{\pi}{2})} = j0.4A = I_L^-$
- Since this is lossless should it be different than the one at the input? Let us see. As you can see they are the same. However, for tests, games etc. we need to show what the question is asking for.
  - $P_{in ave} = \frac{1}{2} V_{in} I_{in}^* = \frac{1}{2} (-40)(-1.6) = 32W = P_{in ave}$
- We can find  $V_g$  how?  $V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}} \rightarrow V_g = V_{in} \frac{Z_g + Z_{in}}{Z_{in}} = -40 \frac{150 + 25}{25} = -280V = V_g$