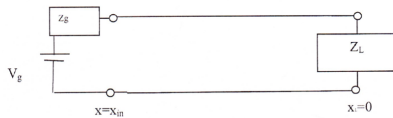


Game 4/24/20 T-line voltage and current

For the following T-line system, you know $Z_L=100$ ohms $Z_0=50$ ohms $Z_g=150$ ohms and the length of the line is $\frac{300\lambda}{4}$

If you know that $V^-(x_{in} = -\frac{300\lambda}{4})$ is 10 volts

- Find V^+ and total I at the input of the line
- Find I^- at the load positions
- Find the average power at the load (Note: In stead sate average power is *realpart of* $\frac{1}{2}VI^*$)
- Can you find V_g ? Explain and show if you can or cannot and find it if you think you can



- To do this the easiest way is to find Z_{in}

$$a. \quad Z_{in} = Z(x_{in} = -\frac{300\lambda}{4}) = Z_0 \frac{1 + \Gamma_L e^{j2\beta(-\frac{300\lambda}{4})}}{1 - \Gamma_L e^{j2\beta(-\frac{300\lambda}{4})}} = 100 \Omega \quad \text{NOTE } \frac{300\lambda}{4} = \frac{150\lambda}{2} \text{ this is integer number of half wavelength}$$

so the exponential will be 1. also

$$b. \quad \Gamma(x_{in} = -\frac{300\lambda}{4}) = \Gamma_{in} = \Gamma_L e^{j2\beta(-\frac{300\lambda}{4})} \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1}{3} \quad e^{j2\beta(-\frac{300\lambda}{4})} = e^{-j2\frac{2\pi}{\lambda}(-\frac{300\lambda}{4})} = 1 \rightarrow \Gamma_{in} = \frac{1}{3}$$

$$c. \quad \Gamma_{in} = \frac{V_{in}^-}{V_{in}^+} \text{ so. } V_{in}^+ = 10(\frac{1}{\frac{1}{3}}) = 30 \text{ V}$$

$$d. \quad I_{in} = \frac{V_{in}}{Z_{in}} = \frac{40}{100} = 0.4 \text{ A} = I_{in}$$

$$b) \quad I_{in}^- = -\frac{V_{in}^-}{Z_0} = -\frac{10}{50} = -0.2 \text{ A} = I_{in}^- \quad I_{in}^+ = \frac{V_{in}^+}{Z_0} = \frac{30}{50} = 0.6 \text{ A} = I_{in}^+$$

- Since this is lossless should it be different than the one at the input? Let us see. As you can see they are the same. However, for tests, games etc. we need to show what the question is asking for.

$$a. \quad P_{in \text{ ave}} = \frac{1}{2} V_{in} I_{in}^* = \frac{1}{2} (40)(0.4) = 8 \text{ W} = P_{in \text{ ave}}$$

$$b. \quad P_{L \text{ ave}} = \frac{1}{2} V_L I_L^* = \frac{V_L V_L^*}{2Z_L^*} = \frac{(40)(0.4)}{2} = 8 \text{ W}$$

$$d) \quad \text{We can find } V_g \text{ how? } V_{in} = V_g \frac{Z_{in}}{Z_g + Z_{in}} \rightarrow V_g = V_{in} \frac{Z_g + Z_{in}}{Z_{in}} = 40 \frac{150 + 100}{100} = 100 \text{ V} = V_g$$