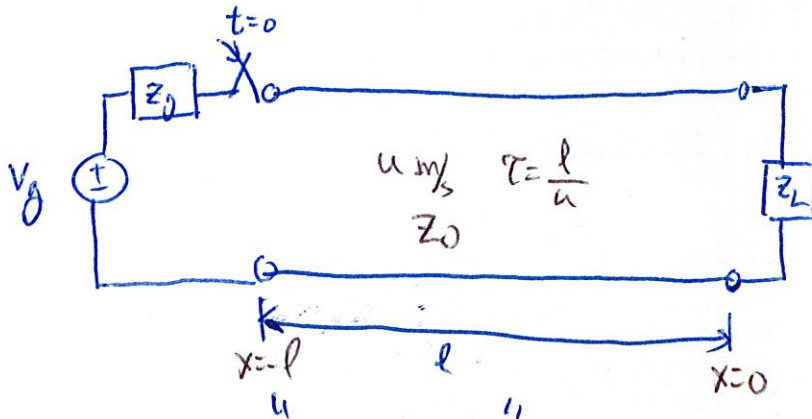


Setting up the problem



⇒ we reach steady state

$t \gg \tau$ "there standing waves of V & I"

Assuming V_g is
as $V_g \cos(\omega t)$ V

* $t=0$ the switch
closes &

* $t \gg \tau$ The bouncing
of the signal
going to the load reflecting
from Z_L
back
reflecting from Z_0
:

• $V(x,t) \rightarrow \underline{V}(x)$ we know these are
 $I(x,t) \rightarrow \underline{I}(x)$ "phasors"

* at any position on the line

$$x=-l \quad \underline{V}(-l) = \underline{V}^+(-l) + \underline{V}^-(-l)$$

Important

Assume lossless line

$$\gamma = j\beta \quad \beta = \frac{2\pi}{\lambda} \text{ of the "wave" on the line } \frac{\omega}{\beta} = u$$

$$\underline{V}(x) = \underline{V}_0^+ e^{-j\beta x} + \underline{V}_0^- e^{+j\beta x}$$

$$\underline{I}(x) = \underline{I}_0^+ e^{-j\beta x} + \underline{I}_0^- e^{+j\beta x}$$

$$Z(x) = \frac{\underline{V}(x)}{\underline{I}(x)}$$

$$\Gamma_V(x) = \text{voltage reflection} = \frac{\underline{V}^-(x)}{\underline{V}^+(x)}$$

$$\Gamma_I(x) = -\Gamma_V(x)$$

$$\underline{I}_0^+ = \frac{\underline{V}_0^+}{Z_0} \quad \underline{I}_0^- = -\frac{\underline{V}_0^-}{Z_0}$$

* what if we know $V_0 = V_g \Rightarrow V_g \cos \omega t$ ✓

To see how to know V & I all along the line we need to have systematic formulation

we can
always
'play'

$$Z(x) = \frac{V(x)}{I(x)} = \frac{V_0^+ e^{-j\beta x} + V_0^- e^{+j\beta x}}{I_0^+ e^{-j\beta x} + I_0^- e^{+j\beta x}} = \frac{V_0^+ e^{-j\beta x}}{I_0^+ e^{-j\beta x}} \frac{1 + \Gamma_0 e^{2j\beta x}}{1 - \Gamma_0 e^{2j\beta x}}$$

But let us be more systematic

$$\Gamma(x) = \frac{V^-}{V^+} = \text{voltage Reflection Coeff} = \frac{V_0^- e^{+j\beta x}}{V_0^+ e^{-j\beta x}} = \Gamma_0 e^{2j\beta x}$$

$$\boxed{\Gamma_v(x) = \Gamma_0 e^{2j\beta x}}$$

$$Z(x) = \frac{V(x)}{I(x)} = \frac{V_0^+ e^{-j\beta x} + V_0^- e^{+j\beta x}}{I_0^+ e^{-j\beta x} + I_0^- e^{+j\beta x}} = Z_0 \frac{1 + \Gamma(x)}{1 - \Gamma(x)}$$

examine this at the load

$$Z(x=0) = Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} \Rightarrow$$

$$\boxed{\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}} \quad \text{We know That}$$

$$\text{So } \Gamma(x=-l) = \Gamma_0 e^{2j\beta(-l)}$$

$$\boxed{\Gamma_{(x=-l)} = \Gamma_0 e^{-2j\beta l}}$$

$$Z(x=-l) = Z_0 \frac{1 + \Gamma(x=-l)}{1 - \Gamma(x=-l)} = Z_0$$